

KATHMANDU UNIVERSITY  
End Semester Examination  
September 2024

Marks Scored:

Level : BIT

Year : I

Exam Roll No. :

Time: 30 mins.

Registration No.:

Course : COMP 105

Semester : I

F. M. : 10

Date :

22 SEP 2024

SECTION "A"

[20Q.  $\times$  0.5 = 10 marks]

*Choose and encircle the most appropriate answer. Symbols have their usual meanings.*

- In analog-to-digital conversion the sequence of operations is
  - Sampling, coding, Quantization
  - Coding, Quantization, Sampling
  - Sampling, Coding, Quantization
  - Quantization, Sampling, Coding
- The binary equivalent of octal number 705 is:
  - 1110101
  - 1010111
  - 111000101
  - 11100101
- If A and B are inputs to the two input X-OR gates, which of the following expressions for output is correct?
  - $\bar{A}B + A\bar{B}$
  - $\bar{A}\bar{B} + A\bar{B}$
  - $\bar{A}B - A\bar{B}$
  - $\bar{A}\bar{B} + AB$
- The NAND gate output will be low if the two inputs are
  - 0 0
  - 0 1
  - 1 0
  - 1 1
- The Boolean expression  $\bar{A}B + A\bar{B} + AB$  is equivalent to
  - $A + B$
  - $\bar{A} + B$
  - $\bar{B} + A$
  - $A \cdot B$
- Which theorem states the following statements?  
 $A + B = B + A$   
 $A \cdot B = B \cdot A$ 
  - Distributive law
  - Associative law
  - Commutative law
  - De-Morgan's Theorems
- Which of the following expressions represents the Boolean function  $F = A + B' C$  in the sum of minterms
  - $F(A, B, C) = \Sigma(0, 2, 3, 4, 5)$
  - $F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$
  - $F(A, B, C) = \Sigma(1, 3, 5, 6, 7)$
  - $F(A, B, C) = \Sigma(2, 4, 5, 6, 7)$
- The number of control lines for an 8-to-1 multiplexer is
  - 2
  - 3
  - 4
  - 5
- A mod-N counter counts up to
  - N
  - 2 N
  - $N-1$
  - $N+1$



KATHMANDU UNIVERSITY  
End Semester Examination  
September 2024

Level : BIT  
Year : I  
Time : 2 hrs. 30 mins.

22 SEP 2024

Course : COMP 105  
Semester : I  
F. M. : 40

SECTION "B"  
[6Q. × 4 = 24 marks]

Attempt *ANY SIX* questions.

1. Briefly discuss the process of analog-to-digital conversion. [4]
2. What do you mean by universal gates? How does a NOR gate act as a universal gate? Discuss the De- Morgan's theorem. [1+2+1]
3. With the function table find the expression for a priority encoder and draw the internal diagram. [4]
4. Draw the block diagram of the four-bit Johnson's counter and discuss its working principle.
5. Design a logic circuit for mod-6 synchronous up-counter and explain the operation using a timing diagram.
6. Draw the internal diagram of the JK flip-flop, and find its truth table and Boolean expression.
7. Find the Boolean expressions for sum, and carry, and construct a logic circuit for a full adder.

SECTION "C"  
[2Q. × 8 = 16 marks]

Attempt *ANY TWO* questions.

8.
  - a. Draw the block diagram of a 3-bit SISO (Serial-In, Serial-Out) shift register and verify its operation for the data "110" with the timing diagram. [2+2]
  - b. Draw the state diagram for the 3-bit UP counter and represent it using a state transition diagram. Assume JK flip-flops have been used. [1+3]
9.
  - a. Design a logic circuit for a 3-bit binary to gray-code converter. Show the truth table and solve using a K-map. [5]
  - b. Simplify the following Boolean function using K-map. [3]  
 $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$   
Which has the don't care conditions  $D(w, x, y, z) = \Sigma(0, 2, 5)$
10.
  - a. Express the Boolean function  $F = A + \bar{B}C$  in a sum of min-terms. [3]
  - b. Convert  $(10AF)_{16}$  into binary and find the octal equivalent of the resulting binary number. [1+2]
  - c. Briefly discuss the categories RAM. [2]

